


Introduction to Computing

Digital Circuits

Jerzy Nawrocki

jerzy.nawrocki@put.poznan.pl
Faculty of Computing & Telecom.
Poznan University of Technology

Conceptual map of the lectures

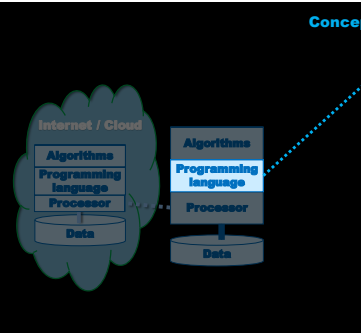


Internet / Cloud

Algorithms
Programming language
Processor
Data

Algorithms
Programming language
Processor
Data

Topic
Imperative Programming
Digital Circuits
Computers
Subprograms
Numerical Methods
Computational Complexity
Object-oriented Programming
Text Processing
Databases and Machine Learning
Parallel Processing
Computer Networks & Cybersec.
Software Engineering
Embedded Systems
Professionalism in Computing

Conceptual map of the lectures

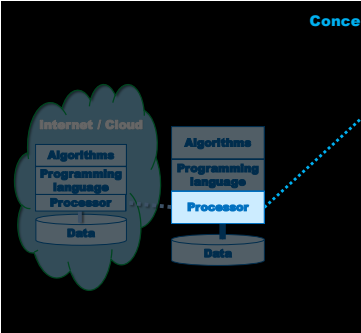


Internet / Cloud

Algorithms
Programming language
Processor
Data

Algorithms
Programming language
Processor
Data

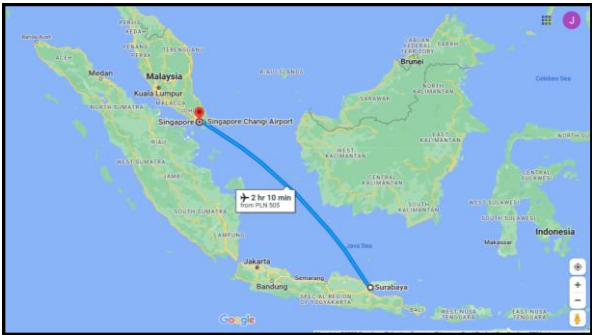Topic
Imperative Programming
Digital Circuits
Computers
Subprograms
Numerical Methods
Computational Complexity
Object-oriented Programming
Text Processing
Databases and Machine Learning
Parallel Processing
Computer Networks & Cybersec.
Software Engineering
Embedded Systems
Professionalism in Computing






Aim of this lecture




What are the main components of contemporary computers?

<https://www.vecteezy.com>


Architecture of IBM PC

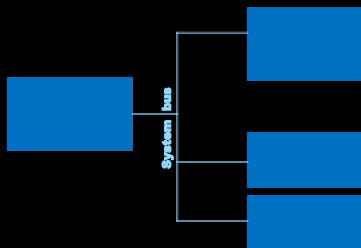

Architecture of IBM PC

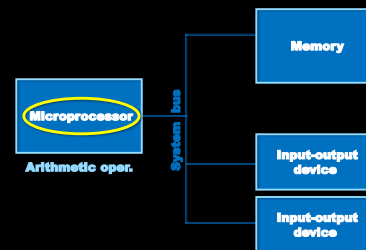


Architecture of a popular microprocessor

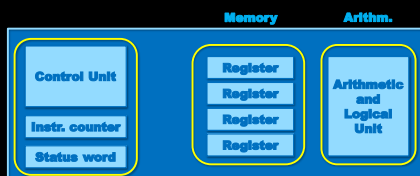

Agenda




- Adders
- Gates

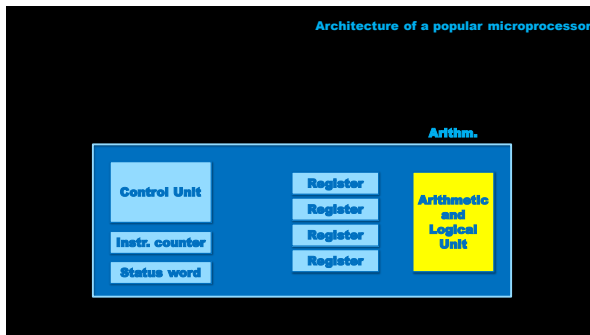


Agenda

- Adders
- Gates
- Register

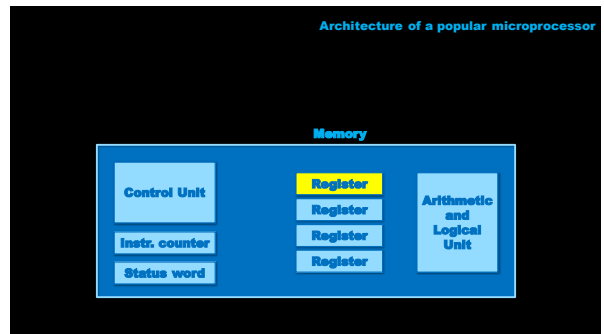

Agenda

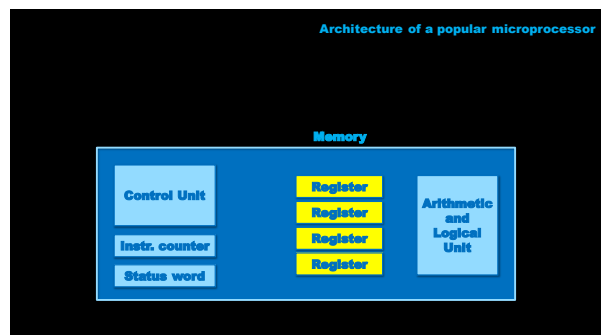
- Adders
- Gates
- Register
- Decoder & multiplexer





Agenda

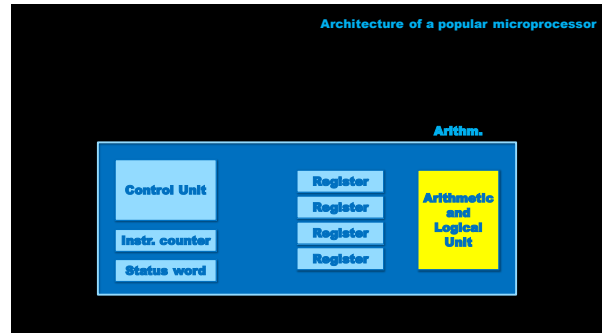- Adders
- Gates
- Register
- Decoder & multiplexer



Decimal arithmetics

101_{10}

$1 \cdot 10^2 + 0 \cdot 10^1 + 1 \cdot 10^0$

$= 100 + 0 + 1$

Decimal arithmetics

101_2


$1 \cdot 2^2 + 0 \cdot 2^1 + 1 \cdot 2^0$

$= 4 + 0 + 1$

Binary arithmetics

Decimal	Binary
0	0
1	1
2	10
3	11
4	100
5	101
6	110
7	111
8	1000

Quiz



Which of the following is the binary representation of decimal number 15?


- a) 11
- b) 111
- c) 1111
- d) 11111

Our problem


How to design a device that would be capable of adding two binary numbers in an automatic way (adder)?




4-bit adder

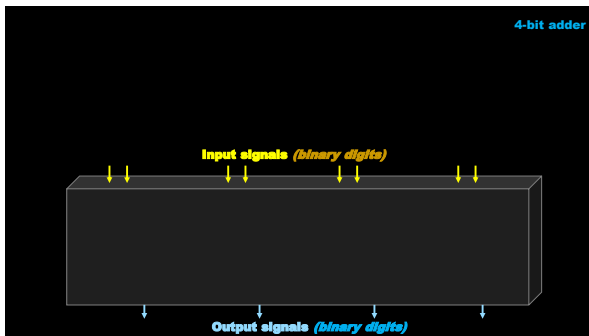

4-bit adder

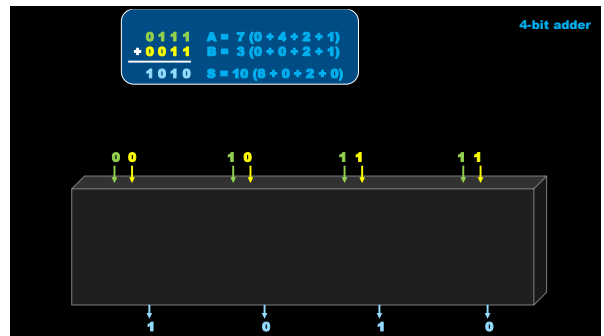

4-bit adder






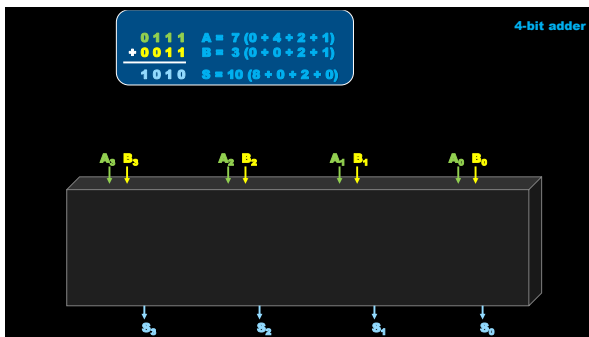







Quiz

What is the decimal result of adding the following binary numbers?


0 1 1 1
+ 0 0 1 1

a) 122₁₀
b) 9₁₀
c) 10₁₀
d) 11₁₀

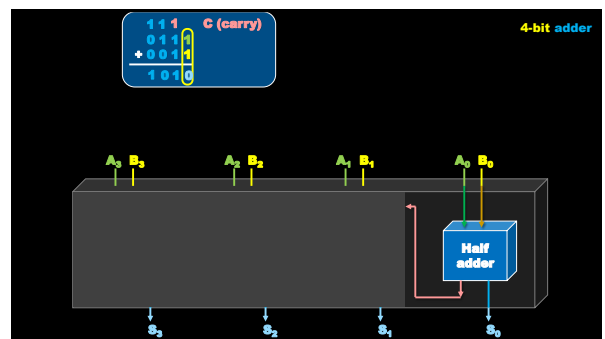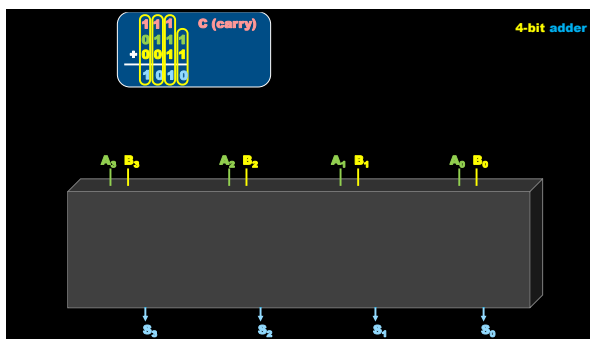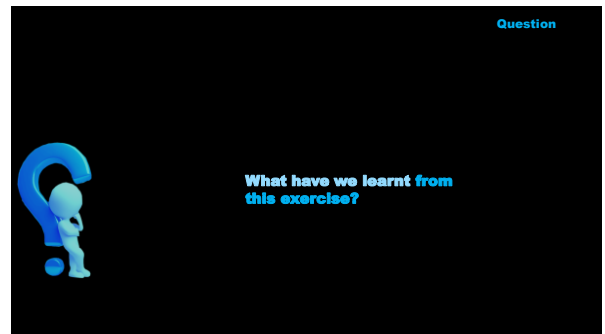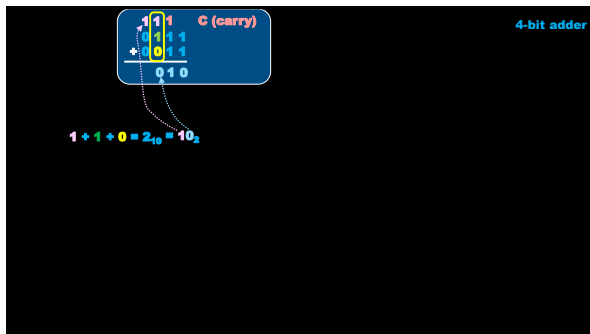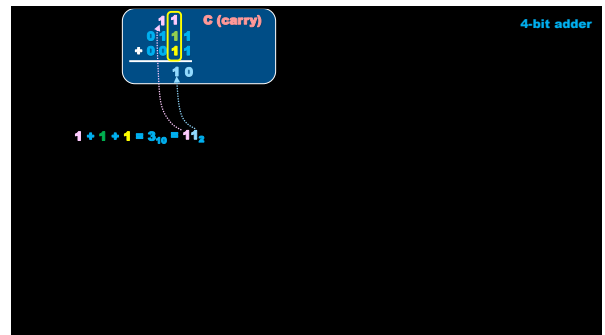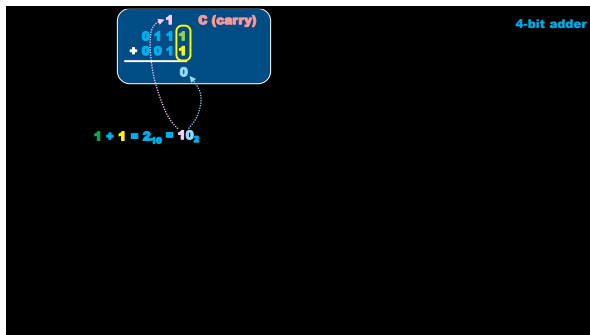

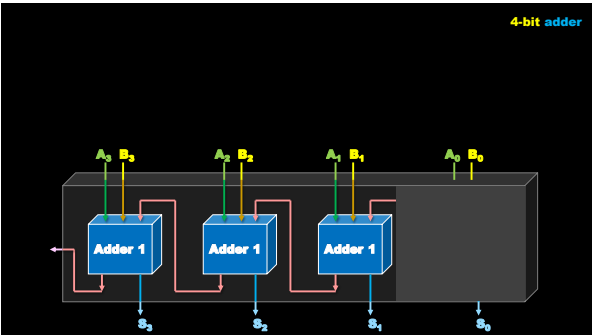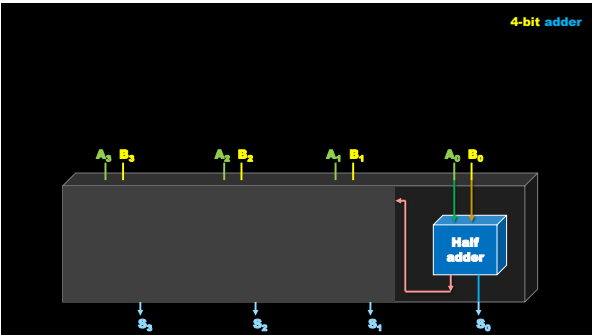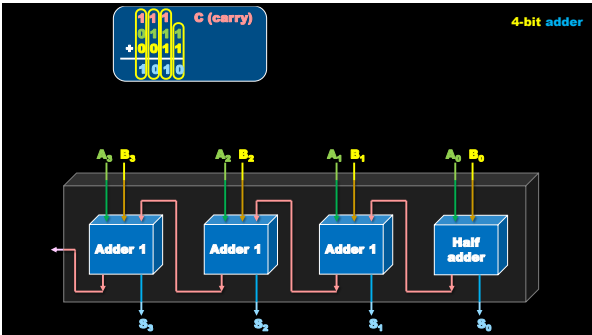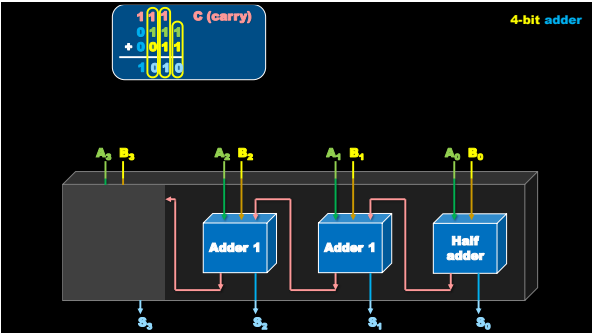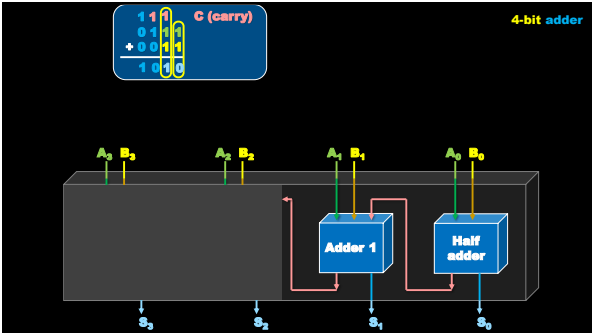

Adder




A	B	C ₀	C ₁	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Agenda




- Adders
- Gates
- Register
- Decoder & multiplexer

Architecture of a popular microprocessor

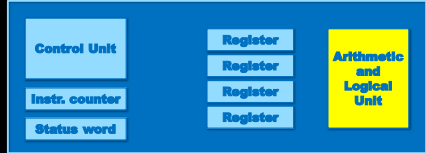

Arithm.

Boolean algebra

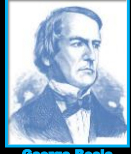


George Boole
1815 – 1864

< {F, T}, T, and, or, not >

A	B	A and B A · B
0	0	0
0	1	0
1	0	0
1	1	1

C: A && B
Python: A and B

Boolean algebra

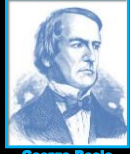


George Boole
1815 – 1864

< {F, T}, T, and, or, not >

A	B	A and B A · B	A or B A + B
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

C: A || B
Python: A or B

Boolean algebra

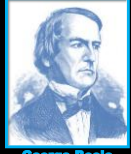

George Boole
1815 – 1864

< {F, T}, T, and, or, not >

A	B	A and B A · B	A or B A + B	not A
0	0	0	0	1
0	1	0	1	1
1	0	0	1	0
1	1	1	1	0

C: ! A
Python: not A

© Jerzy Nawrocki, Introduction to Computing

Boolean algebra




A = 0, 1
B = 0, 1


A and B = $A \cdot B$
not A = $1 - A$
A or B = $A + B$
A or B = $A + B - A \cdot B$

George Boole
1815 – 1864

Application of Boolean algebra



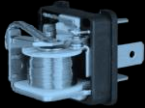0·0 = 0
0·1 = 1·0 = 0
1·1 = 1
0+0 = 0
0+1 = 1+0 = 1
1+1 = 1




Shannon, C. E. (1938).
A symbolic analysis of relay and switching circuits.
Electrical Engineering, 57(12), 713-723.
(Also his master's degree thesis, MIT, 1937)


Claude Shannon
1916 – 2001

<https://www.shannon.com/>

Application of Boolean algebra

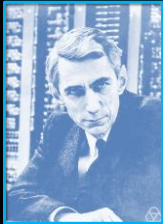

0·0 = 0
0·1 = 1·0 = 0
1·1 = 1
0+0 = 0
0+1 = 1+0 = 1
1+1 = 1






Shannon, C. E. (1938).
A symbolic analysis of relay and switching circuits.
Electrical Engineering, 57(12), 713-723.
(Also his master's degree thesis, MIT, 1937)

Claude Shannon
1916 – 2001

<https://www.pngwing.com/>

Transistor









A replica of the first transistor
invented in Bell Labs in 1947

Transistor PNP **Transistor NPN**

<https://upload.wikimedia.org/wikipedia/commons/b/bf/Replica-of-first-transistor.jpg>

Gates






Jack Kilby
1923 – 2005
Nobel Prize, 2000

Robert N. Noyce
1927 – 1990
Father of Intel

Kilby's original integrated circuit
Texas Instruments, Sep. 12, 1958

Gates


< {F, T}, T, not, and, or >

Jack Kilby
1923 – 2005
Nobel Prize, 2000

Robert N. Noyce
1927 – 1990
Father of Intel

Gates

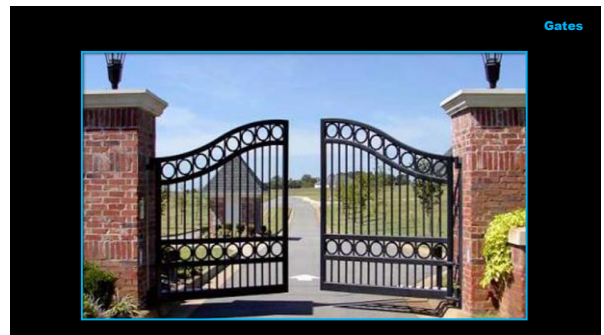

Gates

Gates

Multi-input gates

Boolean algebra


$\langle \{F, T\}, \text{and, or, not} \rangle$

A	B	A and B
0	0	0
0	1	0
1	0	0
1	1	1

$\text{AND}(x_1, x_2, x_3, \dots) = 1 \iff \text{EVERY } x_i = 1$

Boolean algebra

< {F, T}, T, and, or, not >




George Boole
1815 - 1864


A	B	A or B
0	0	0
0	1	1
1	0	1
1	1	1

$OR(x_1, x_2, x_3, \dots) = 0 \equiv \text{EVERY } x_i = 0$



Collector of signals




Collector of signals



Quiz





This is what we need.




This is what we have.

NAND gate






NAND gate

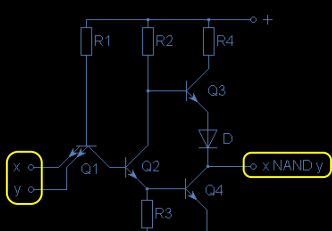


TTL technology (Transistor-Transistor Logic)
Texas Instruments, 1962

7400 Quad 2-input NAND Gates

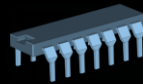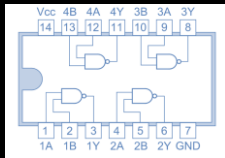

<https://www.pngwing.com/en/free-png-xxdnu/download>

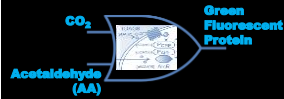Gas-controlled biochemical gates: OR, AND



CO ₂	AA	GFP
0	0	0
1	0	0
0	1	0
1	1	1

Austlander, David, et al.
 "A synthetic multifunctional mammalian pH sensor and CO₂ transgene-control device."
Molecular cell 55.2 (2014): 297-306.

Quiz



This is what we need.



This is what we have.

Propositional calculus



Augustus De Morgan
 1806 - 1871


De Morgan Theorems:

$\text{not}(p \text{ and } q) = \text{not } p \text{ or } \text{not } q$
 $\text{not}(p \text{ or } q) = \text{not } p \text{ and } \text{not } q$

Distribution principles:







$p \text{ and } (q \text{ or } r) = (p \text{ and } q) \text{ or } (p \text{ and } r)$
 $p \text{ or } (q \text{ and } r) = (p \text{ or } q) \text{ and } (p \text{ or } r)$



4-bit adder

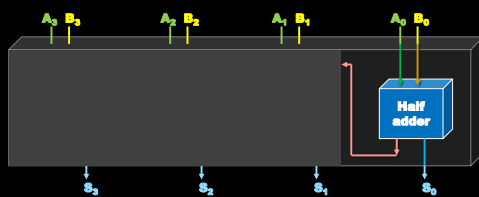

Half adder




A ₀	B ₀	C ₀	S ₀
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

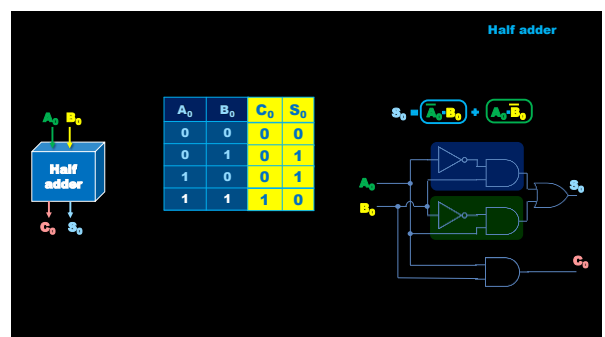
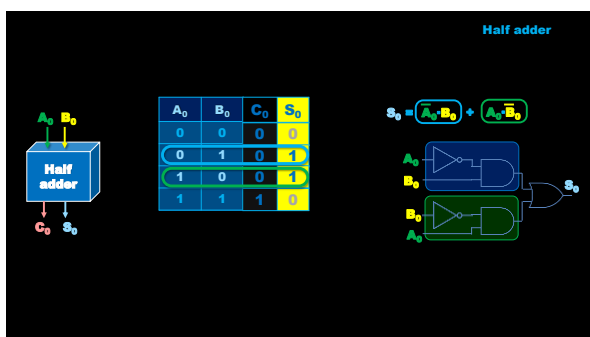
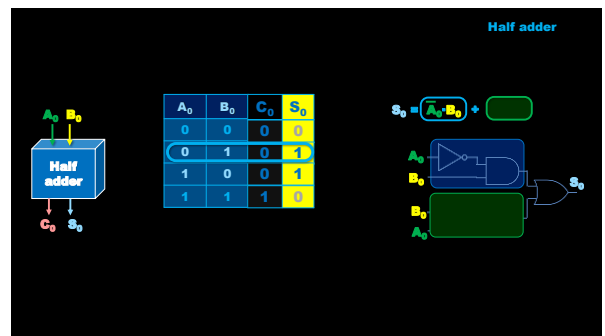
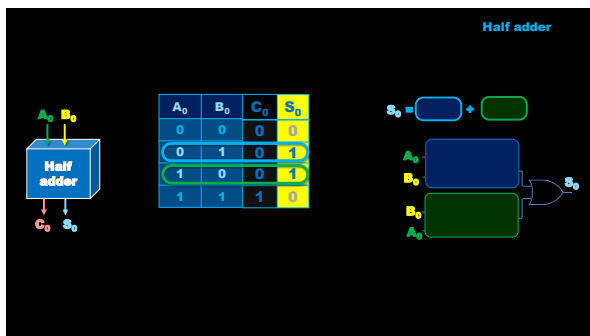
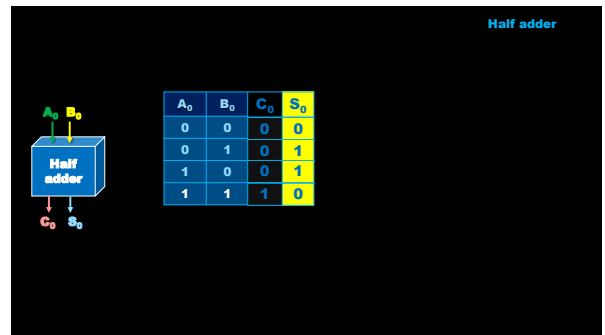
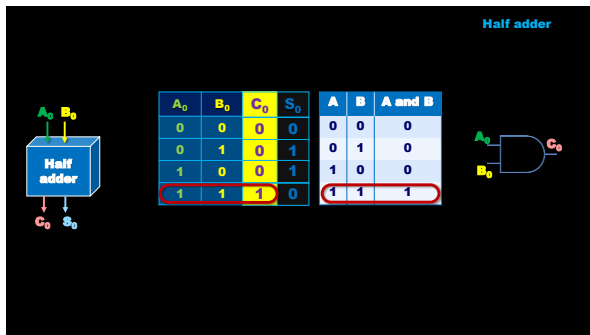






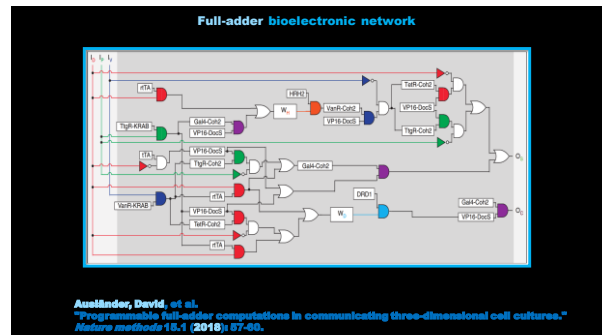
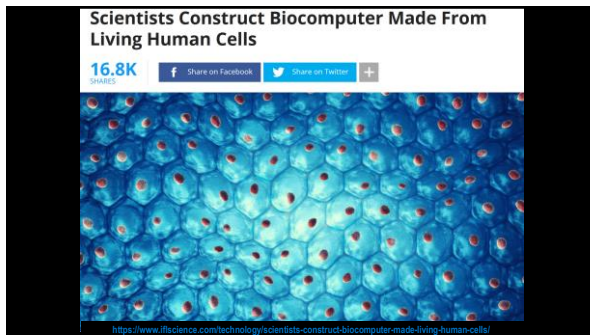








Agenda

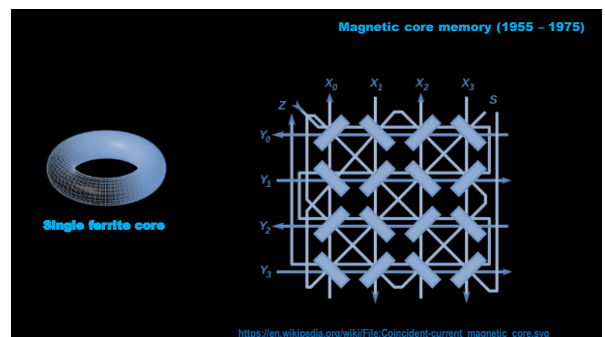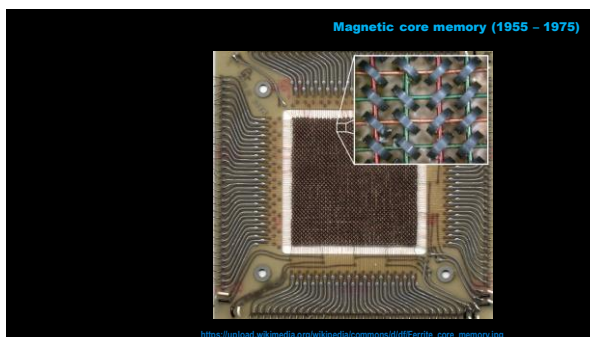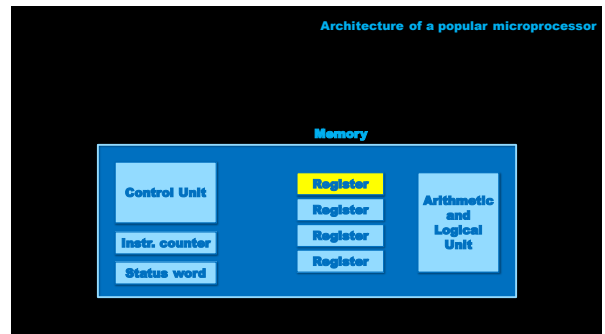- Adders
- Gates
- Register
- Decoder & multiplexer



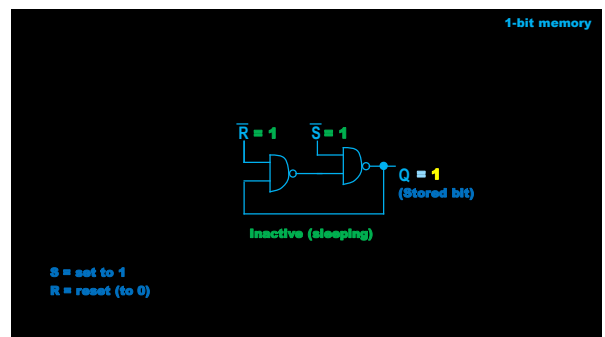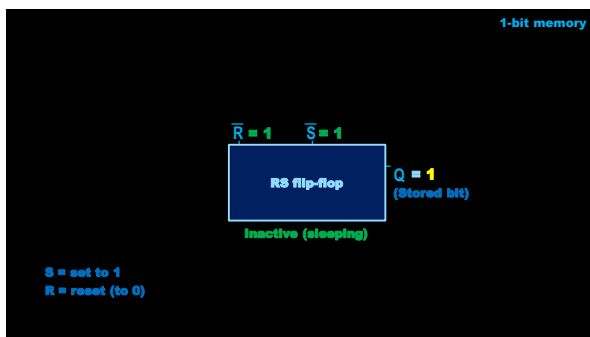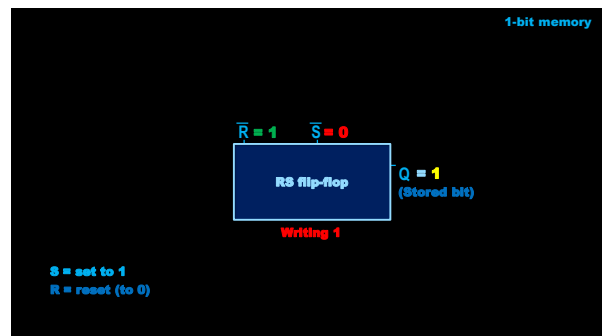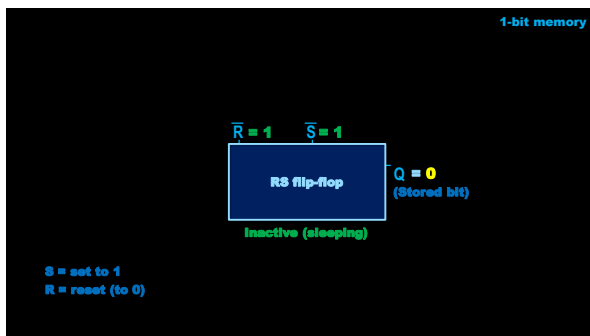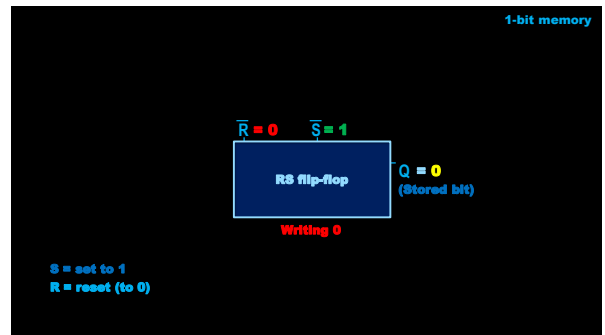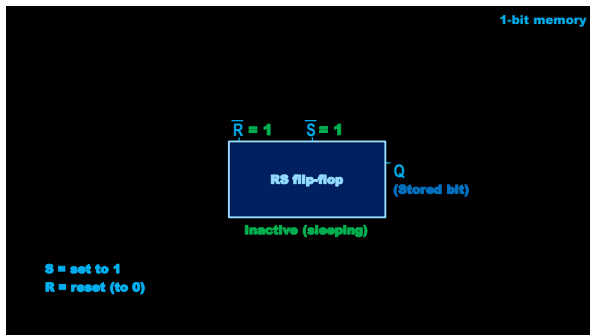

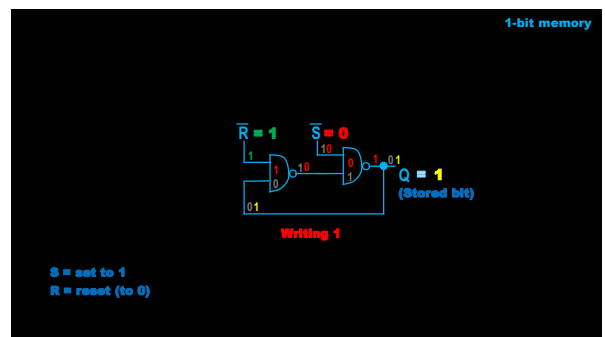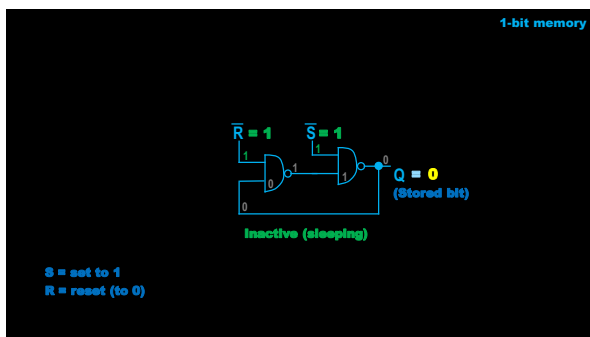
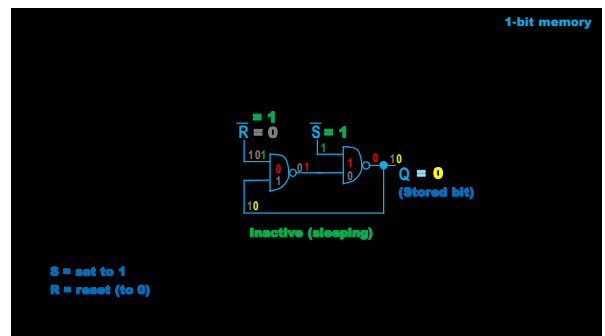
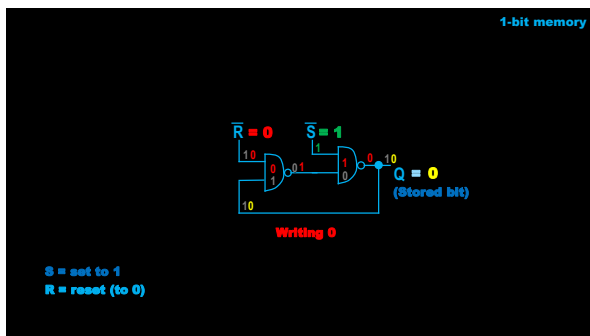
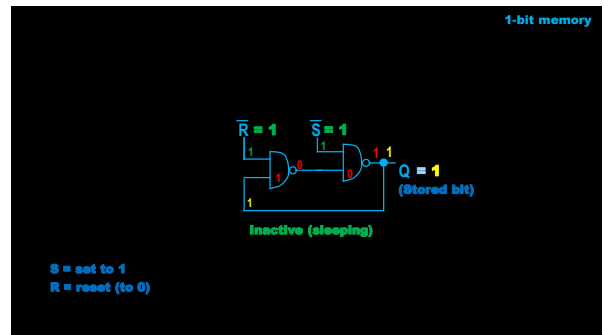
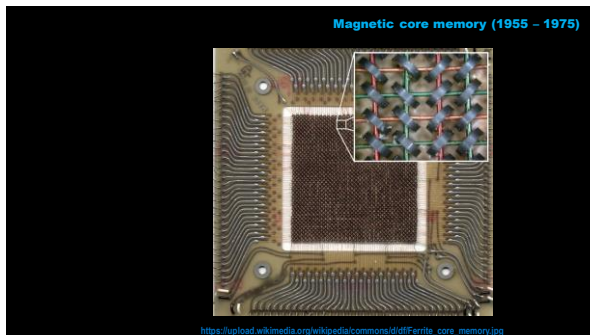


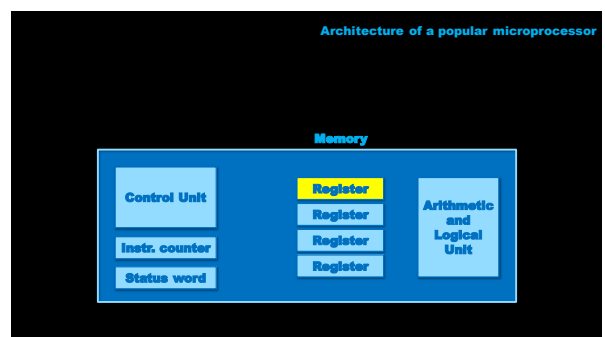
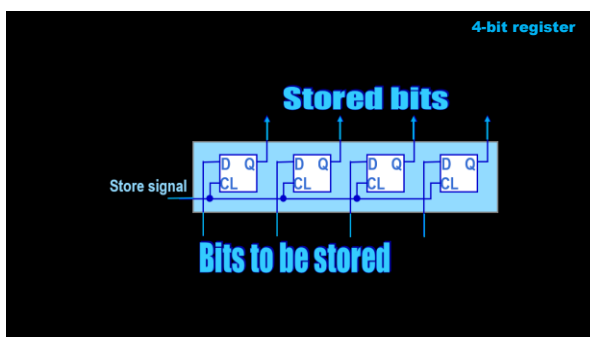
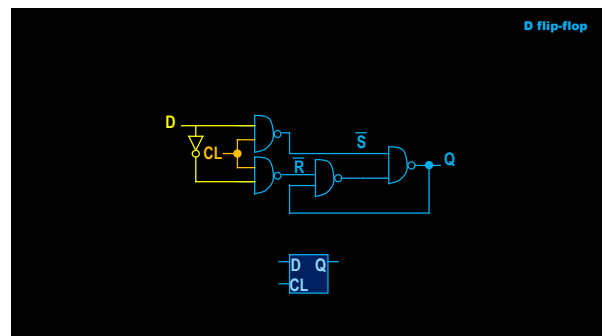
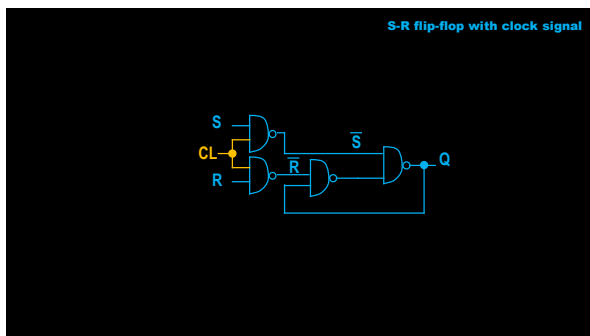
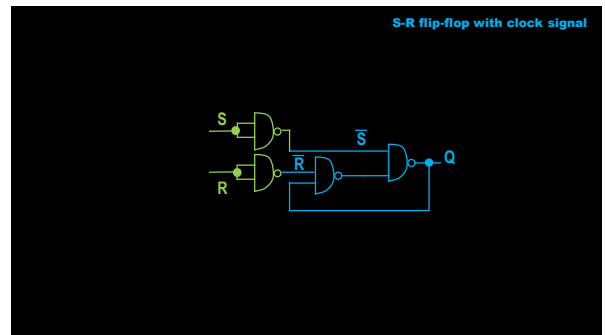
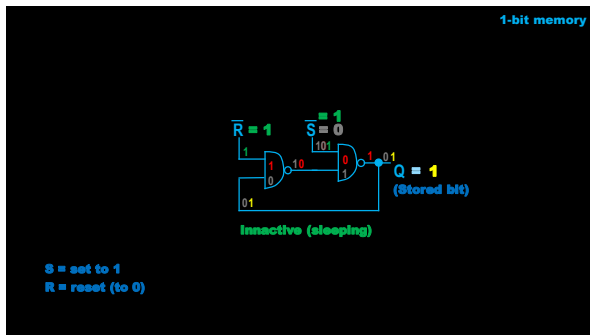








Agenda

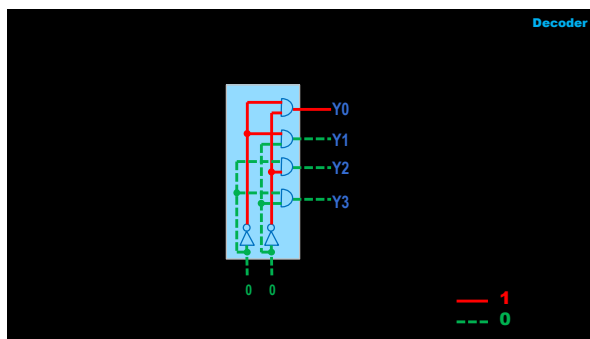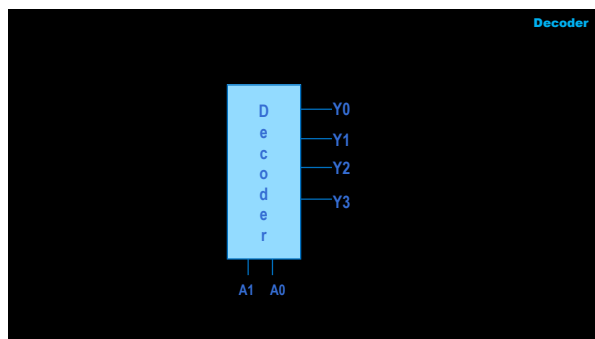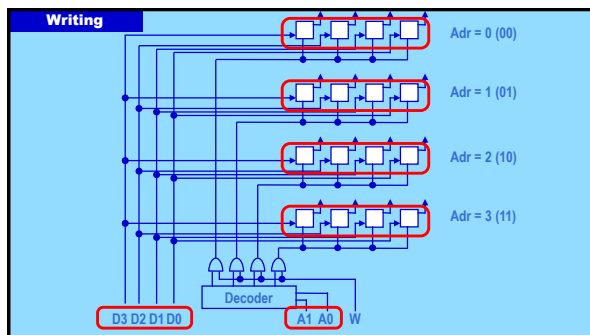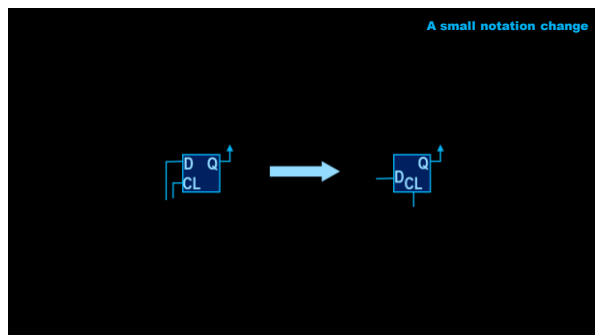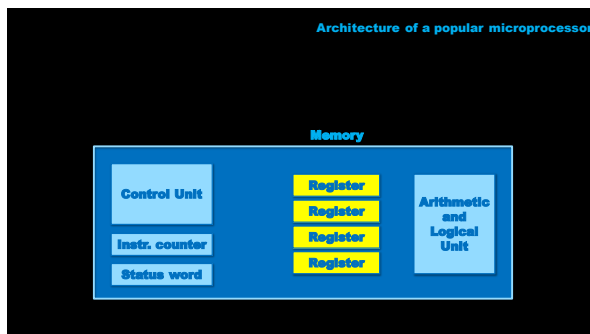
- Adders
- Gates
- Register
- Decoder & multiplexer



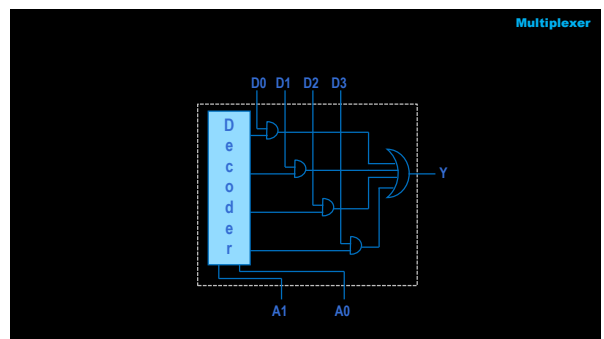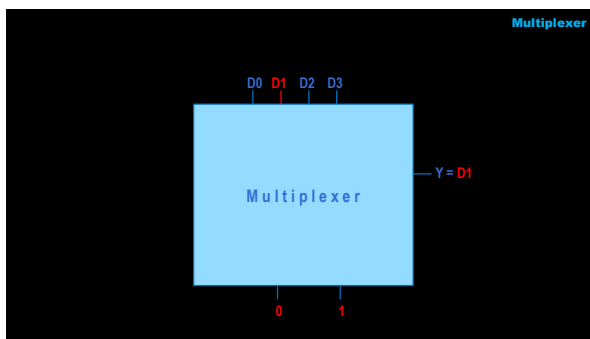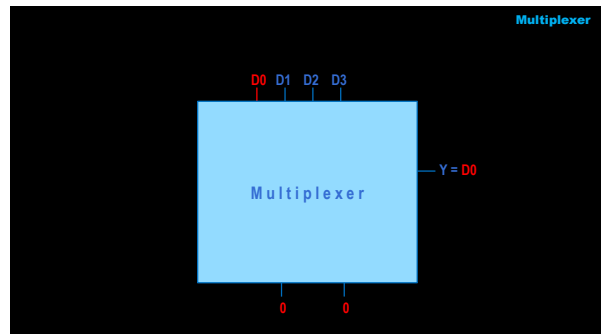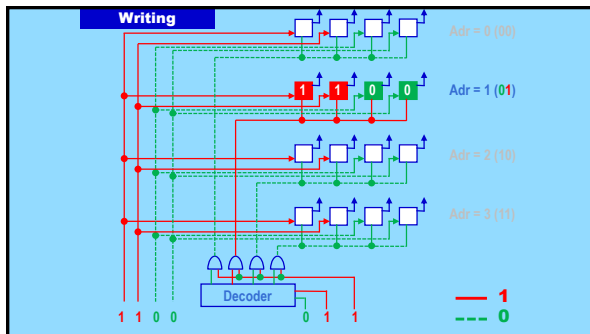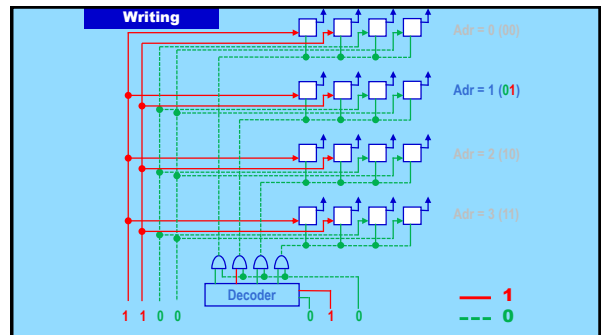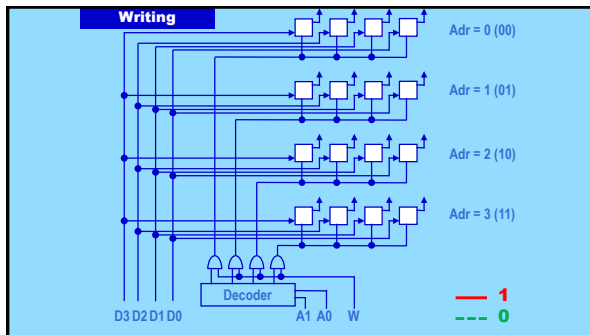

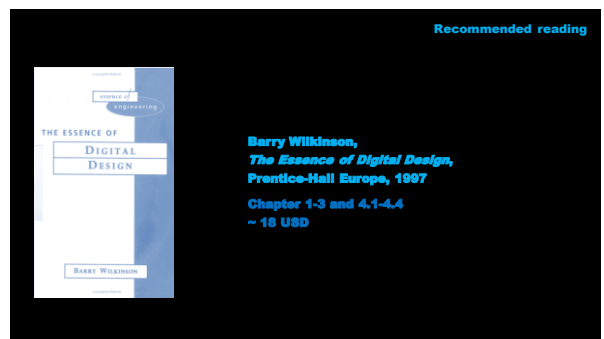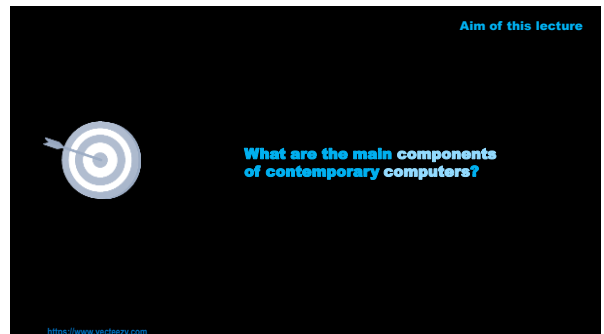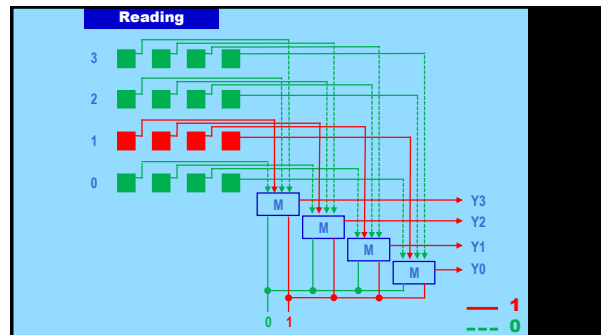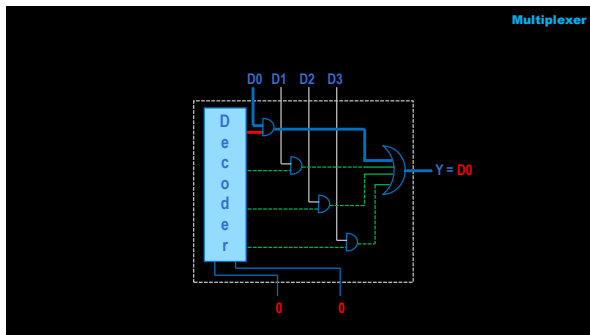

Recommended reading

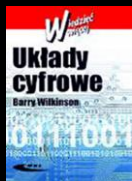

Barry Wilkinson,
Układy cyfrowe,
Wydawnictwa Komunikacji i Łączności, 2003
Rozdz. 1-3 oraz 4.1-4.4
~ 45 zł

Thank you for your attention!



<https://pngtree.com/>

Conceptual map of the lectures

